

* on cherche $S_1 S_3$

$$\begin{aligned} S_1 S_3 &= KE \left(\cos \left(\theta + \frac{4\pi}{3} \right) - \cos \left(\theta + \frac{2\pi}{3} \right) \right) \\ &= KE \left(\cos \theta \cos \frac{4\pi}{3} - \sin \theta \sin \frac{4\pi}{3} - \cos \theta \cos \frac{2\pi}{3} + \sin \theta \sin \frac{2\pi}{3} \right) \\ &= KE \left(\cos \theta \left(-\frac{1}{2} + \frac{1}{2} \right) + \sin \theta \left(\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} \right) \right) \end{aligned}$$

$$S_1 S_3 = KE \sin \theta \sqrt{3} \quad \text{OK}$$


on sait que $E = 115 \text{ V}$ $K_T = 0,45$

$$S_1 S_3 = 115 \times 0,45 \times \sqrt{3} \times \sin \theta \approx 89,6 \sin \theta \quad \text{OK}$$

* on cherche aussi $S_2 S_3$ et $S_2 S_1$

on sait que $S_1 S_3 = KE \sin \theta \sqrt{3} \approx 89,6 \sin \theta$
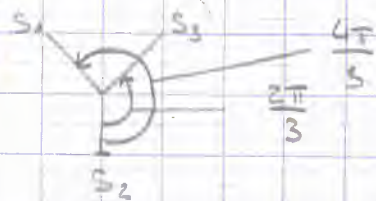
$$\begin{aligned} S_1 S_2 &\approx 89,6 \sin \left(\theta + \frac{4\pi}{3} \right) = U_{12} = V_{S_1 - S_2} \\ S_2 S_3 &\approx 89,6 \sin \left(\theta + \frac{2\pi}{3} \right) \end{aligned}$$



* Vérifier la somme de $S = S_3 S_2 + S_2 S_1 + S_2 S_3 = 0$

$$S = 89,6 \left(\sin \theta + \sin \left(\theta + \frac{4\pi}{3} \right) + \sin \left(\theta + \frac{2\pi}{3} \right) \right)$$


$$S = 89,6 \left(\sin \theta + \sin \theta \cos \frac{4\pi}{3} + \cos \theta \sin \frac{4\pi}{3} + \sin \theta \cos \frac{2\pi}{3} + \cos \theta \sin \frac{2\pi}{3} \right)$$

$$S = 89,6 \left(\sin \theta \left(1 + \cos \frac{4\pi}{3} + \cos \frac{2\pi}{3} \right) + \cos \theta \left(\sin \frac{4\pi}{3} + \sin \frac{2\pi}{3} \right) \right)$$

$$S = 89,6 (0 + 0)$$

$$S = 0 \quad \text{OK}$$

on étudie A2

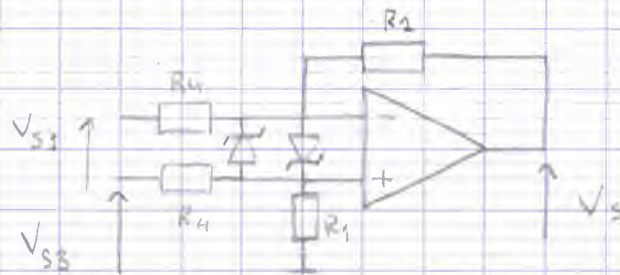

on cherche V_+ $\Rightarrow$ pont div de tension

$$V_+ = V_{31} \cdot \frac{R_1}{R_1 + R_4}$$

$$V_- = \frac{\frac{V_{31}}{R_4} + \frac{V_3}{R_1}}{\frac{1}{R_4} + \frac{1}{R_1}}$$

$$= \frac{V_{31} R_1 + V_3 R_4}{R_4 + R_1}$$

$$V_+ = V_- \Rightarrow V_{31} \cdot \frac{R_1}{R_1 + R_4} = \frac{V_{31} R_1 + V_3 R_4}{R_4 + R_1}$$

$$V_{31} R_1 = V_3 R_1 + V_3 R_4$$

$$V_3 = \frac{R_1 (V_{31} - V_3)}{R_4}$$

$$V_3 = \frac{R_1}{R_4} V_{31} = \frac{R_1}{R_4} 90 \sin \theta$$

$$V_3 = \frac{R_1}{R_4} (V_{31} - V_3)$$

OK

$$V_3 = 90 \sin(90) \cdot \frac{11}{500}$$

$$= 1,5 V$$

$$V_3 = 90 \sin(90) \cdot \frac{R_1}{R_4} = 1,5 V$$


comme $\Rightarrow 90 \sin 90^\circ \quad \theta = 90^\circ$

on a $R_1 = 11 K \Omega \quad R_4 = 500 K$

$$* U_{31} = 90 \sin \theta \cos(\omega t) = V_3 - V_1$$

$$* U_{12} = 90 \sin(\theta + \frac{4\pi}{3}) \cos \omega t = V_1 - V_2$$
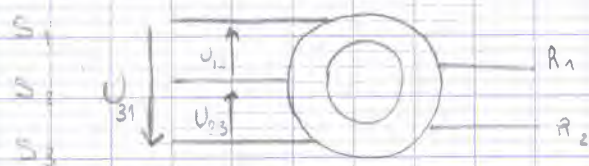
$$* U_{23} = 90 \sin(\theta + \frac{2\pi}{3}) \cos \omega t = V_2 - V_3$$



pour A3 :

Pont div $V_1 = V_2 \cdot \frac{R_2}{R_1 + R_2}$ $V_2 = V_{2GND}$

$$a V_{NGND} - V_{GNGN} - V_{NG}$$

$(a-2) V_{NGND}$

$$a=2$$

$$V_1 = \frac{R_3 V_3 + R_2 (V_3 + V_1)}{2R_2 + R_3} = \frac{\frac{1}{R_3} + \frac{V_1}{R_3} + \frac{V_3}{R_2}}{\frac{2}{R_3} + \frac{1}{R_2}}$$

$$V_5 = \frac{R_2}{R_3} \left(V_{2GND} (2R_2 + R_3) \cdot \frac{1}{R_1 + R_2} (V_{3GND} + V_{1GND}) \right)$$

$$= \frac{R_2}{R_3} \left[a V_{2N} - V_{3N} - V_{1N} \right] + (a-2) V_{NGND}$$

$a = \frac{1}{\frac{2R_2 + R_3}{R_1 + R_2}}$

$$= \frac{R_2}{R_3} K E \left(a \cos \theta - \cos(\theta + \frac{2\pi}{3}) - \cos(\theta + \frac{4\pi}{3}) \right)$$

$$= \frac{R_2}{R_3} K E \left(a \cos \theta + \frac{1}{2} \cos \theta + \frac{\sqrt{3}}{2} \sin \theta + \frac{1}{2} \cos \theta - \frac{\sqrt{3}}{2} \sin \theta \right)$$

$$= \frac{R_2}{R_3} K E (a+1) \cos \theta = \frac{R_2}{R_3} 3(a+1) \cos \theta$$

$K E V_3 = V_{s11}$

$$1 - R_1 \sin \theta \sin \theta$$

$$2R_1 + R_3 = 2$$

$$I_B = \frac{V_{CC} - V_{CE}}{R_2 + R_3} \approx \frac{V_{CC}}{R_2 + R_3}$$

$$I_B = \frac{R_1}{R_4} \cdot I_E \approx \frac{R_1}{R_4} \cdot I_C$$

$$I_C = \frac{V_{CC}}{R_2 + R_3}$$

$$I_B = \frac{R_1}{R_4} \cdot I_C$$

$$V_{CE} = \frac{R_2}{R_2 + R_3} \cdot V_{CC}$$

$$V_{CE} = \frac{R_1 R_3}{R_2 R_4 (a+1)} \cdot \tan \theta$$


$$a = \frac{1}{R_4 + R_2} (2R_2 + R_3)$$

$$V_{S1/N} = K E \sin \theta$$

$$V_{S2/GND} = K E \sin \theta + V_{NGND}$$

$$V_{SGND} = \frac{R_1}{R_4} [V_{S2/GND} - V_{S1/GND}]$$
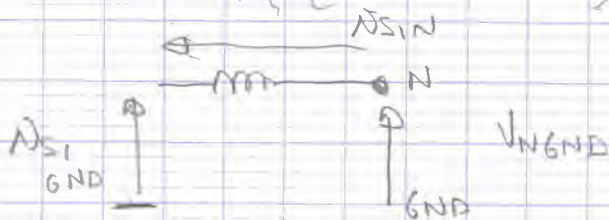
$$= \frac{R_1}{R_4} [K E \sin \theta + V_{NGND} - K E \cos(\theta + \frac{\pi}{2}) - V_{NGND}]$$



$$V_{S1/GND} - V_{S2/GND} = (V_{S1/N} + V_{NGND}) - (V_{S2/N} + V_{NGND})$$

$$= V_{S1/N} - V_{S2/N}$$